




Current Sources & Resistance

Capacitors as a source

- Suppose a conductor was placed in a charged capacitor, connecting the two charged plates. What would happen?
 - The electrons will move from the negative side to the positive side
- This movement of electrons is called electric current.

Electric Current

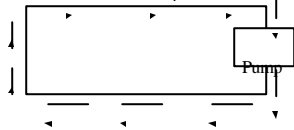- Flow of electrical charge
 - flows between two points of different potential



- maintained by a type of charge pump, which continuously changes the potential

Sources of Current

- Electromagnetic Induction
 - Moving a magnetic field
- Photoelectric Effect
 - Emission of electrons when illuminated
- Thermoelectric
 - Two different metals attached at two junctions, each junction at a different temperature

Sources of Current

- Piezoelectric
 - Crystals subjected to mechanical stress
- Chemical
 - Primary
 - Reactants are used up
 - Storage Cell
 - Reaction is reversible

Moving Charge

- Charges are not created or destroyed, only transferred from one side of the pump to the other
 - Ampere
 - amount of charge moved in a circuit every second
- 1 C/s = 1 Amp
- measured with an ammeter


$$I = \frac{q}{t}$$

Resistance

- The opposition to the flow of electric charge
- In a wire: $R = r \frac{L}{A}$
 - ? = resistivity
 - L = Length
 - A = Area (cross-sectional)
- Resistor
 - Carbon granules are mixed with varying amounts of clay can be molded into cylinders having a finite resistance.


Electric Circuit Diagrams

- Symbols

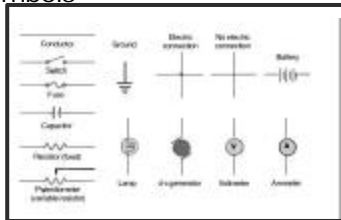

Dry Cell

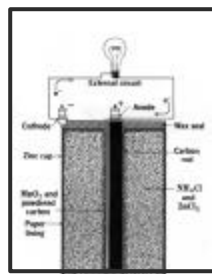- Primary Parts
 - Electrolyte
 - Anode (+)
 - Cathode (-)
- Emf (ξ)
 - Electromotive force
 - Amount of energy supplied by the cell for each unit of charge on the electrodes



Internal Resistance

- The resistance of the battery itself
- Causes the terminal voltage to drop when the battery is connected in a circuit.
- Depends on the electrolyte, the electrode material and the age of the battery
- Very small impact on the circuit and will be ignored in building circuits

Combining Cells in Series

- The emf (V) of the cells is the sum of the emfs of the individual cells
- The current in each cell and in the external circuit is the same throughout
- The internal resistance of the battery is the sum of the internal resistances of the individual cells




Combining Identical Cells in Parallel

- The emf is equal to the emf of each separate cell
- The total current in the circuit is divided equally among the cells
- The reciprocal of the internal resistance of the battery is equal to the sum of the reciprocals of the internal resistance of the cells



Resistors

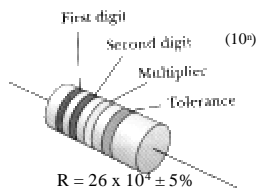

Color	Number	Tolerance
Black	0	
Brown	1	
Red	2	
Orange	3	
Yellow	4	
Green	5	
Blue	6	
Violet	7	
Gray	8	
White	9	
Gold		5%
Silver		10%

Ohm's Law of Resistance

- The ratio of the emf of the source to the current in the circuit is constant.
- This constant is the resistance in the circuit.

$$\frac{V}{I} = R$$

Return to Honors Physics Notes
