

# Capacitors

---

---

---

---

---

---

---

---

## Capacitors

- Used to store a set amount of charge
- made of two conductors separated by an insulator
- measured in farads (F)
- most commercial capacitors are usually  $10 \times 10^{-12}$  F to  $500 \times 10^{-6}$  F

$$C = \frac{Q}{V}$$

---

---

---

---


---

---

---

---

## Capacitors

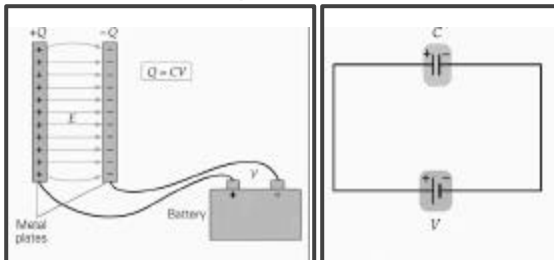

(a) Parallel-plate capacitor

(b) Schematic circuit diagram

---

---

---

---

---

---

---

---

## Factors affecting Capacitance

- Area of plates
- Distance between plates
- Material between plates
  - Example: paper, air, vacuum

---

---

---

---

---

---

---

---

## Capacitors

- Capacitance of a parallel – plate capacitor (in air).

$$C = \frac{\epsilon_0 A}{d}$$

Permittivity  
of free space =  $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/(\text{N} \cdot \text{m}^2)$

- Energy in a charged capacitor

$$U_c = \frac{1}{2} QV = \frac{Q^2}{2C} = \frac{1}{2} CV^2$$

---

---

---

---

---


---

---

---
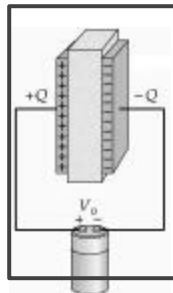
## Dielectrics

- The material used in capacitors to increase the amount of charge stored on the plates.
  - Example: paper or plastic
- Keeps plates from coming into contact with each other.
- Each material has a specific value (K)



---

---

---

---

---

---

---

---

## Dielectric Constant

- The capability of a capacitor to store charge depends on the material, and is characterized by the dielectric constant (K).
- P. 528 has a chart of some constants.
- K is dimensionless, and always greater than 1.
- Values are comparisons with vacuum values.

---

---

---

---

---

---

---

---

## Dielectric Effect On Capacitance

- If we designate the vacuum values as  $E_0$  and  $V_0$ , then the dielectric constant is defined as

$$K = \frac{V_0}{V} = \frac{E_0}{E}$$

- The dielectric increases the capacitance by a factor of K:

$$C = \frac{Q}{V} = KC_0$$

---

---

---

---

---

---

---

---

## Capacitors in Series

- When capacitors are wired in series, the charge ( magnitude Q ) is the same on all the plates.
  - $Q = Q_1 = Q_2 = Q_3 = \dots$
- The sum of the voltage drops add up to the voltage source.
  - $V = V_1 + V_2 + V_3 + \dots$

---

---

---

---

---

---


---

---
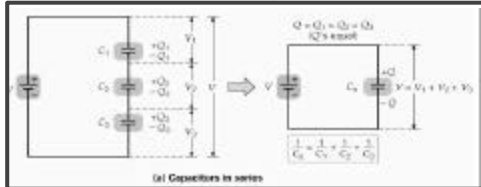
## Equivalent Series Capacitance

- The value of a single capacitor that could replace the series combination.

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$




---

---

---

---

---

---

---

---

## Capacitors In Parallel

- The voltage across parallel capacitors are the same.
  - $V = V_1 = V_2 = V_3 = \dots$
- Total stored charge is equal to the sum of the individual charges.
  - $Q_{\text{total}} = Q_1 + Q_2 + Q_3 + \dots$

---

---

---

---

---

---


---

---

## Equivalent Parallel Capacitance

- The equivalent capacitance to parallel capacitors is the sum of the individual capacitances.

$$C_p = C_1 + C_2 + C_3 + \dots$$

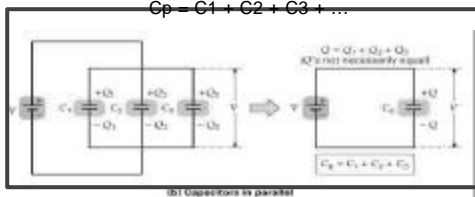


---

---

---

---

---

---

---

---