



Series Circuits

1



Circuits

- Electrical Circuit


- A set of electrical components that are connected to provide one or more paths for moving charges
- A closed electrical loop in which charge can flow
- Must have a high potential (Voltage) and low potential (Voltage) for current to flow

2

Circuit Safety

- **Short Circuit**

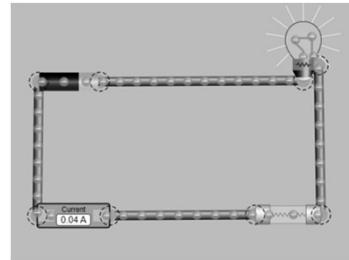- A circuit with little or no resistance.



- **Fuse**

- A piece of metal that melts when the current in the circuit becomes too great.

- **Circuit Breaker**

- A resettable switch that opens when the current in a circuit reaches a set value.

3


Voltage and Circuits

- Voltage is the energy per unit charge supplied by the source of electrical current.
- Any battery or generator is a voltage source.
- A voltage source must be connected to a circuit to produce a current in the circuit.
- Each element in a circuit “uses up” some of the voltage supplied. This is called a voltage drop.

4

Series Circuits

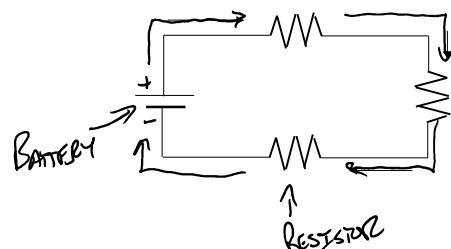- Circuits in which there is only one path for the current to take.



5

General Rules for Series Circuits


- The current in all parts of the circuit is the same (Constant Current)
- The sum of all the ~~separate~~ voltage drops is equal to the applied voltage (Voltage adds up)
- The total resistance in a series circuit is equal to the sum of the individual resistances
- Ohm's Law can be used for any resistor, or for the entire circuit.

$$V = IR$$

6

Kirchoff's Second Law

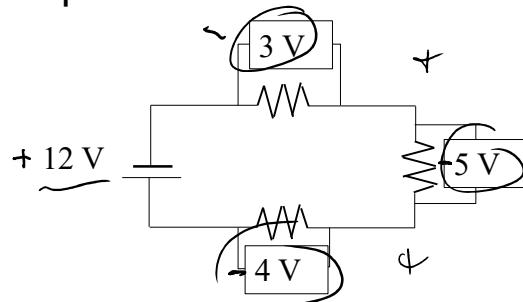
- The sum of all changes in potential in a complete circuit is equal to zero



7

Equivalent Resistance (Series)

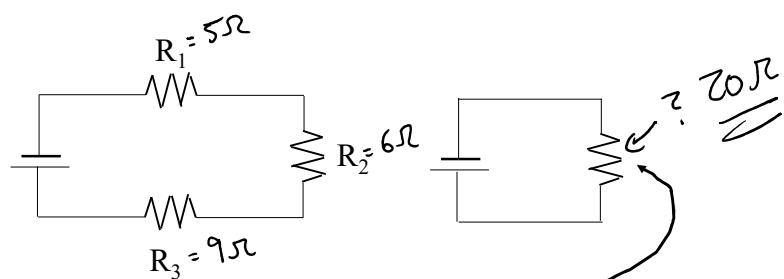- A single resistor that can be placed in a circuit in place of all other resistors in the circuit



$$R_{\text{eq(series)}} = R_1 + R_2 + R_3 + \dots$$


8

Sample Problem

- A 9.0 V battery is connected to four light bulbs, as shown in the picture. Draw a schematic of the circuit.

- What is the equivalent resistance in the circuit?
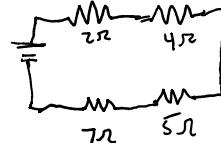
$$2\Omega + 4\Omega + 7\Omega + 5\Omega = 18\Omega$$




- What is the current in the circuit?

$$V = IR \Rightarrow I = \frac{V}{R} = \frac{9V}{18\Omega} = 0.5A$$


- What is the voltage dropped across each light?

	V	I	R
Batt	9V	0.5A	18Ω
R ₁	2V	0.5	2Ω
R ₂	4V	0.5	4Ω
R ₃	5V	0.5	5Ω
R ₄	3.5V	0.5	7Ω

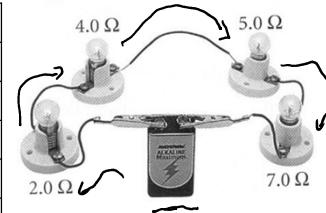

9

Sample Problem

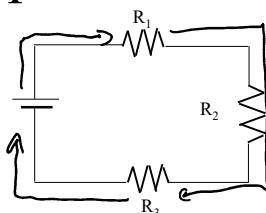

	V	I	R
Batt	144.0 V	3.0 A	48Ω
R ₁	72V	3.0A	24Ω
R ₂	27V	3.0 A	9Ω
R ₃	45V	3.0 A	15Ω

$$45V + 72V + 27V = 144V$$

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

$$48\Omega = 24\Omega + 15\Omega + 9\Omega$$

10